

Op-Amp as inverting and non-inverting Amplifier.

Aim:- To study Op-Amp as inverting and non-inverting amplifier.


Material required:

- i) Multimeter
- ii) Breadboard
- iii) CRO
- iv) Function generator for input source.
- v) Power Supply ($\pm 15V$)
- vi) Op-Amp (IC-741) - 1NO
- vii) Resistors $R_{in} = 1k$, $R_f = 3.9k, 5.6k$

Theory:-

An operational amplifier (op-amp) is a very high gain differential amplifier with input impedance and low output impedance. The basic circuit made using a difference amplifier having two input and one output. The plus (+) input produces an output that is in phase with the signal applied, whereas an input to the minus (-) input results in an opposite polarity output.

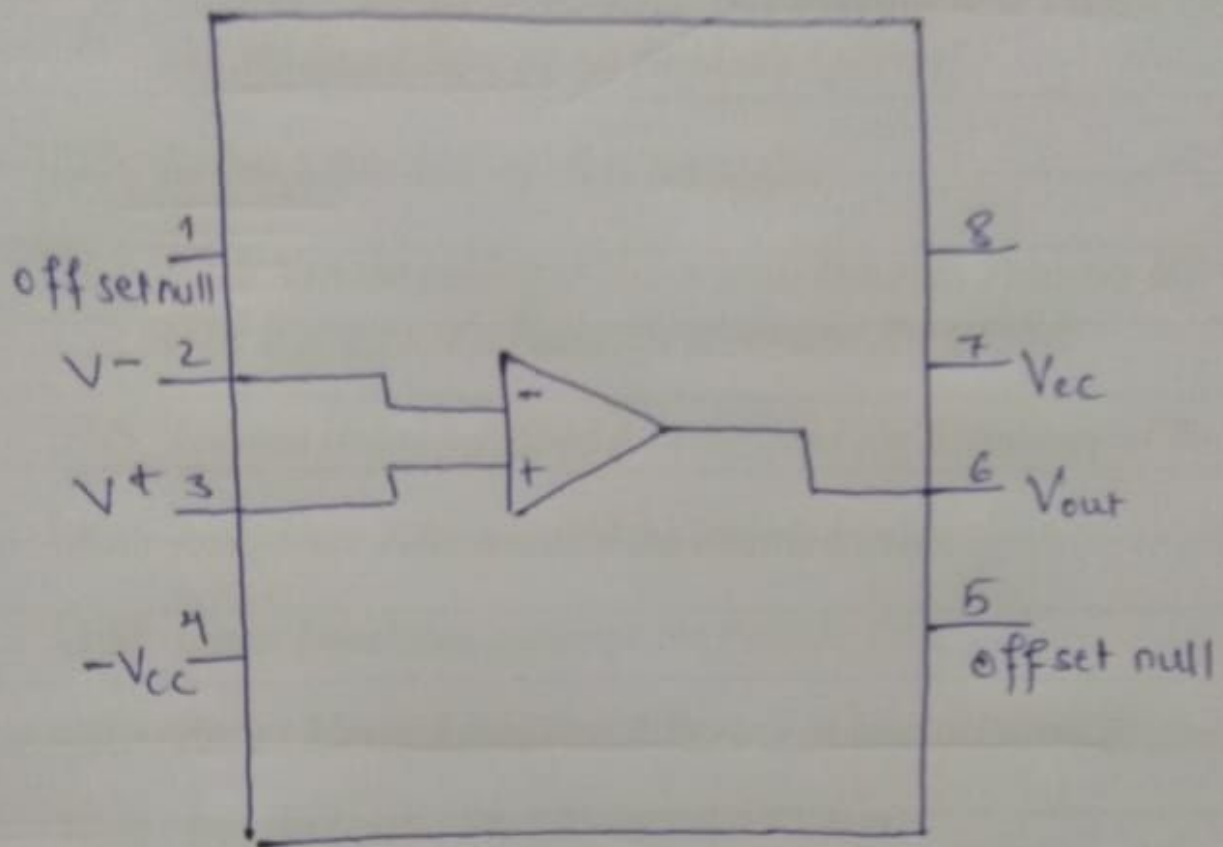Most exciting op-amp's are produced on a single semi-conductor substrate as an integral circuit (IC 741). The two most widely used constant gain amplifiers are the inverting and non-inverting amplifiers.



[Fig - Operational Amplifier (Op-Amp)]

Inverting Amplifier.

It inverts and amplifies a voltage (multiplied by a negative constant)

$$V_{out} = -\frac{R_f}{R_{in}} V_{in}$$

$Z_{in} = R_{in}$ (because V_- is a virtual ground)

Non-Inverting Amplifier.

It amplifies a voltage (multiplies by a constant greater than 1)


$$V_{out} = V_{in} \left(1 + \frac{R_2}{R_1} \right)$$

input impedance $Z_{in} \approx \infty$ (infinity).


1. The input impedance is at least the impedance between non-inverting (+) and inverting (-) inputs, which is typically $1\text{ M}\Omega$ to $10\text{ T}\Omega$, plus the impedance of the path from the inverting (-) input to ground (i.e. R_1 in parallel with R_2)
2. Because negative feedback ensures that the non-inverting and inverting inputs match, the input impedance is actually much higher.

PROCEDURE:

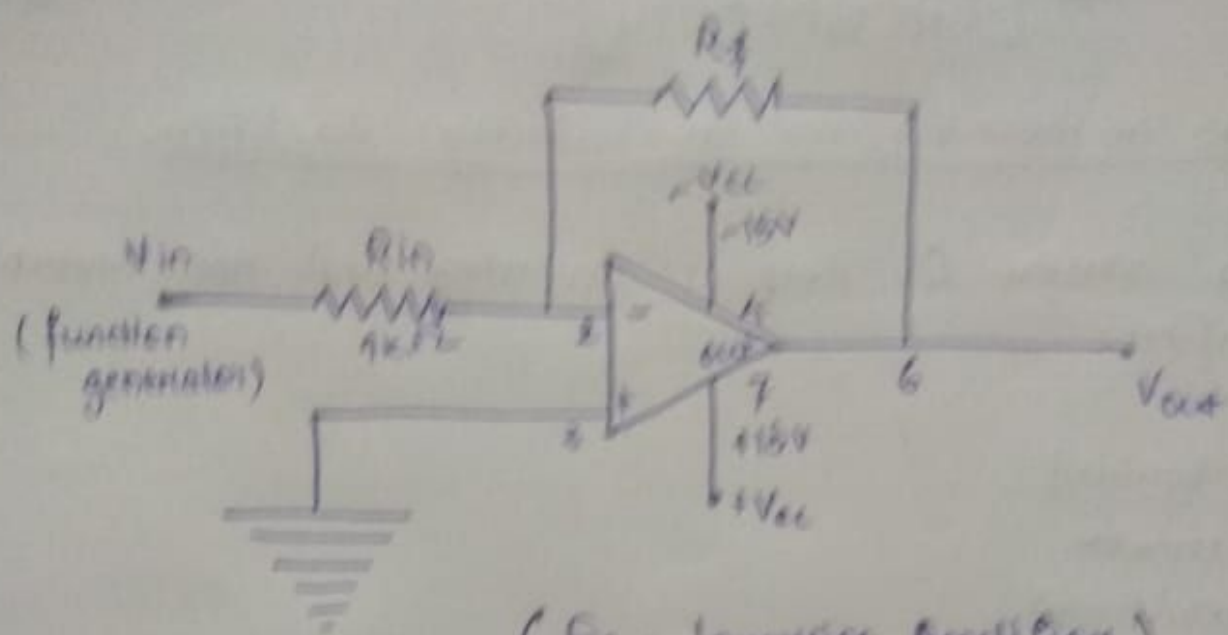- 1) The Op-Amp was setup as per the circuit diagram (inverting or non-inverting as the case may be).



(Fig - Inverting Amplifier)

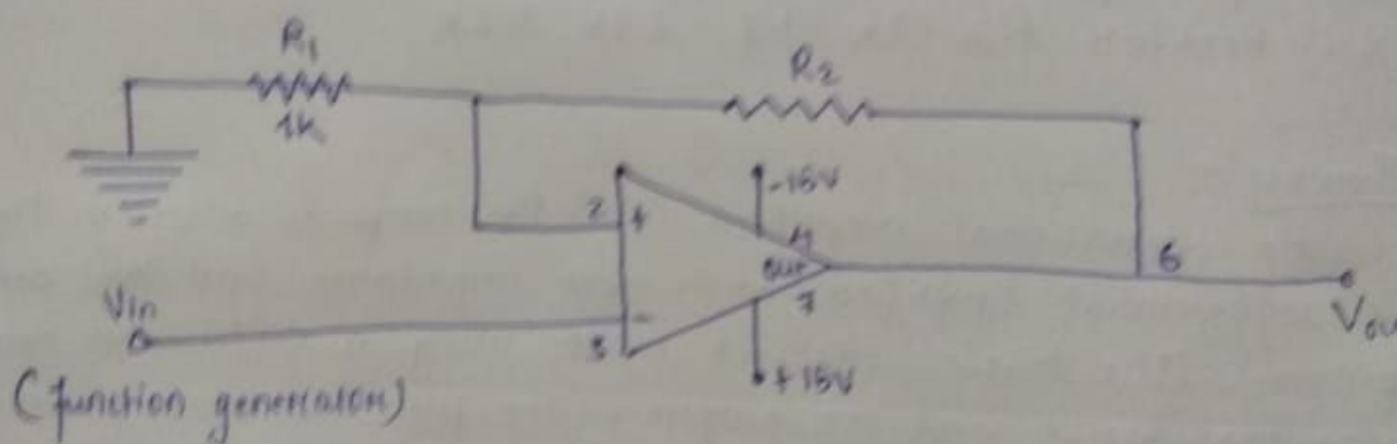

(Fig - Non-Inverting Amplifier)

2. Power supply was provided and the gain of the amplifier was measured by noting down the output voltage with a multimeter.
3. The gain was determined with the value of feedback resistor (R_f) keeping the input resistance constant (R_{in}).


Observation Table :

$$R_f = 3.9 \text{ k}\Omega, f = 1 \text{ kHz}$$

Type of Amplifier	Input AC Voltage	Output Voltage	Calculated Theoretical gain	Measured practical gain	Measured phase difference
Inverting	1V	4V	-3.9	-4	180°
Non-inverting	1V	5.52V	4.9	5.52	0°


For $R_f = 5.6 \text{ k}\Omega$, we only have calculated theoretical gain from the gain formula for inverting and non-inverting input. So we have gain for inverting input and non-inverting input are -5.6 and 6.6 respectively.

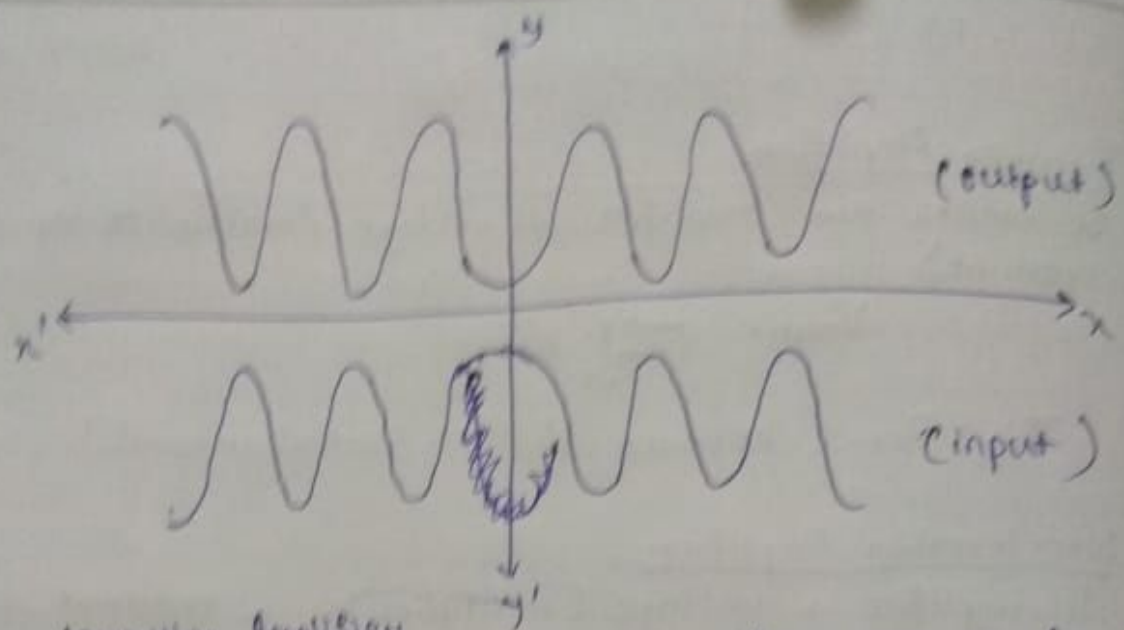CONCLUSION: In this experiment, we came to know about the principle and characteristics of an operational amplifier. We also learnt about its application as an inverting and non-inverting amplifier, their characteristics and working. Both the type of amplifier have a wide range of application in field of electronics.



Inverting Amplifier
 Input Voltage = 1V
 Output Voltage = 4V (observed)
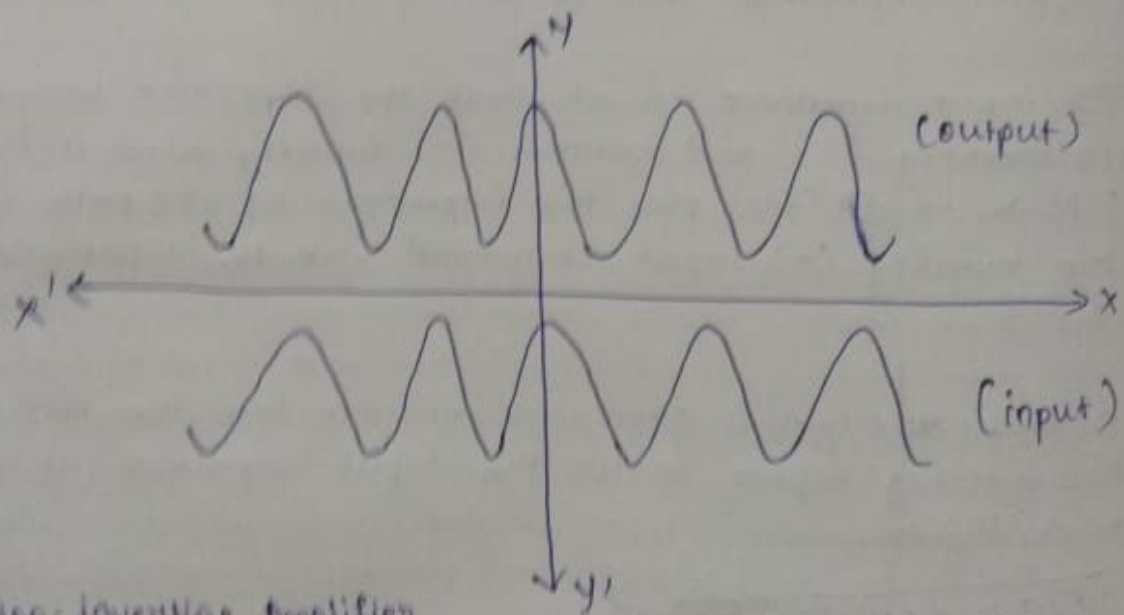
$$R_f = 3.9 \text{ k}\Omega, f = 2 \text{ kHz}$$



Non-Inverting Amplifier
 Input Voltage = 1V
 Output Voltage = 5.52V
 (observed)

$$R_f = 3.9 \text{ k}\Omega, f = 1 \text{ kHz}$$